



Name: \_\_\_\_\_

Sec: \_\_\_\_\_

Score:

Question 1 \_\_\_\_\_ of possible 4 points

Question 2 \_\_\_\_\_ of possible 4 points

Question 3 \_\_\_\_\_ of possible 5 points

Question 4 \_\_\_\_\_ of possible 2 points

Total \_\_\_\_\_ of possible 15 points

Answer the following questions:

**Question 1: [4 pts.]**

1. The voltage and current expressions that were measured on a lossless transmission line are:

$$v(z, t) = 20 \cos(2\pi \times 10^8 t - \pi z + \pi/6) + 10 \cos(2\pi \times 10^8 t + \pi z)$$

$$i(z, t) = 0.4 \cos(2\pi \times 10^8 t - \pi z + \pi/6) - 0.2 \cos(2\pi \times 10^8 t + \pi z)$$

- a. (1 pt.) Determine the voltage phasor.


- b. (1 pt.) Determine the current phasor. How could you physically interpret the minus sign?

- c. (1 pt.) Determine the reflection coefficient at the load.

- d. (1 pt.) Determine the impedance of the load.

**Question 2: [4 pts.]**

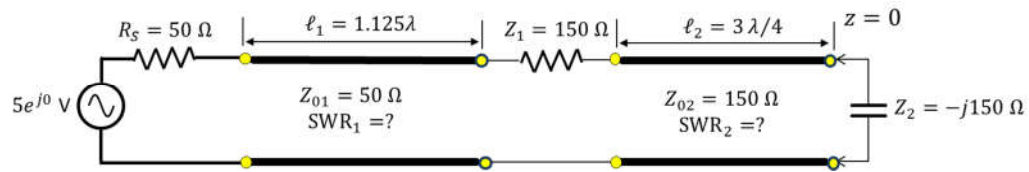
2. Consider the transmission line circuit below. Assume lossless lines.



- a. (2 pts.) Find the standing wave ratio on each line.
- b. (2 pts.) Find the time-average power delivered to each impedance  $Z_1 = 150 \, \Omega$  and  $Z_2 = j150 \, \Omega$ .

**Question 3: [5 pts.]**

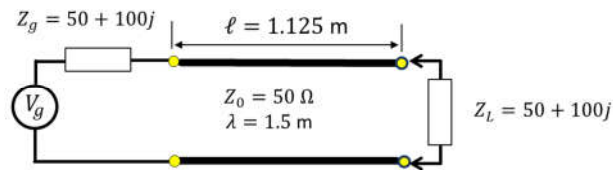
3. Consider the transmission line circuit below. Assume lossless line.



- (1 pt.) Find  $Z_{in}$  using the Smith chart and show the constant standing wave ratio (SWR) circle.
- (1 pt.) Find the power delivered to the load in terms of  $V_g$ .
- (1 pt.) Find the position of the current maximum nearest the load using Smith chart.
- (2 pts.) What minimum length of the transmission line will give maximum power delivery to  $Z_L$ ? Explain (use Smith chart). Find the maximum power delivered to the load in terms of  $V_g$ .

**Question 4: [2 pts.]**

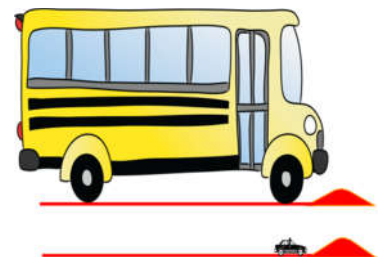- I. (1 pt.) What does this picture represent?



- II. (1 pt.) Most RF and microwave instruments and coaxial cables have standardized impedance of  $50 \Omega$ . Briefly state why?