



## ECE 323 - Microwave Engineering Problem Set #3

### Smith Chart

[P1] Use the Smith chart to find the following quantities for a T-line with  $Z_0 = 50 \Omega$ ,  $f = 600 \text{ MHz}$ , and  $Z_L = 60 + j50 \Omega$ . The speed of propagation on the T-line is  $c$ .

- (a) The reflection coefficient at the load.
- (b) The reflection coefficient at a distance of 20 m from the load toward the generator.
- (c) Input impedance at 20 m from the load.
- (d) The SWR on the line.
- (e) The distance from the load to the first voltage maximum and first voltage minimum.
- (f) The distance from the load to the first current maximum and first current minimum.
- (g) The load admittance.

[P2] Repeat **P1** on Problem set #2 using Smith chart.

[P3] **2.21**- Use the Smith chart to find the shortest lengths of a short-circuited  $75 \Omega$  line to give the following input impedance:

- (a)  $Z_{in} = 0$ .
- (b)  $Z_{in} = \infty$ .
- (c)  $Z_{in} = j75$ .
- (d)  $Z_{in} = -j50$ .
- (e)  $Z_{in} = j10$ .