



Menoufia University
Faculty of Electronic Engineering
Electronics and Electrical Communications Eng. Dept.
Third Year – Spring 2018
ECE 323 - Microwave Engineering
Problem Set #4



Impedance Matching

- [P1] A load impedance $Z_L = 25 + j30$ is to be matched to a $50\ \Omega$ line using an L-section matching networks at the frequency $f=1$ GHz.
- Find two designs using smith chart (also plot the resulting circuits).
 - Verify that the matching is achieved for both designs.
 - List the drawbacks of matching using L network.
- [P2] A T-line with $Z_0 = 50\ \Omega$ is terminated with $Z_L = 60 + j50\ \Omega$ as shown in **Fig. P2**.

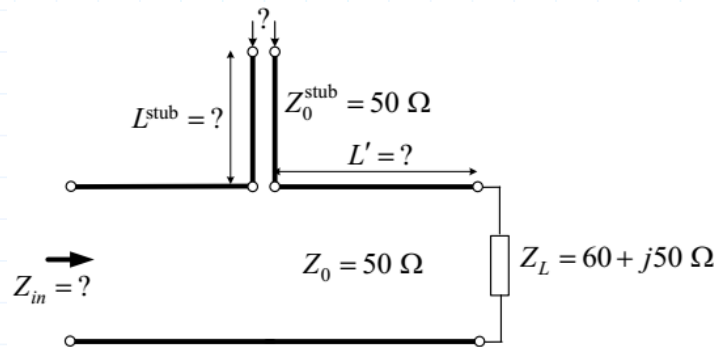


Fig. P2: Circuit for Problem P2.

- Find the length L' (in terms of λ) of the piece of this T-line such that at $L = L'$ the real part of the input impedance Z'_{in} satisfies $\Re\{Z'_{in}\} = Z_0$. What is $\Im\{Z'_{in}\}$ at this position?
- Use a short-circuited series stub of a $50\text{-}\Omega$ to cancel $\Im\{Z'_{in}\}$ connected at L' as shown in **Fig. P2**. What is the length of the stub L^{stub} ?
- What is now the input impedance Z_{in} at $L = L'$?
- Repeat part (b) using an open-circuited stub?