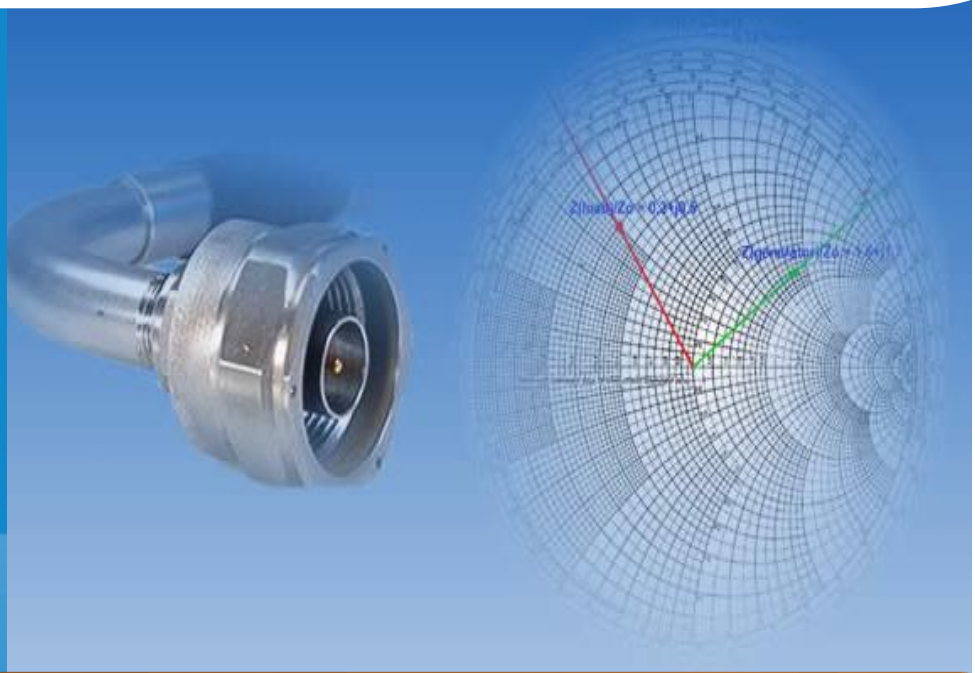


# Lecture 8

# T-Line Matching

EE221

Electromagnetic Field  
Theory (2-B)  
Spring 2020



**Dr. Ahmed Farghal**

Assistant Professor

Dept. of Electrical Engineering,  
Faculty of Engineering, Sohag University

**29/03/2020**

# Impedance Matching

- **Impedance matching** (simply **matching**) one portion of a circuit to another is an immensely important part of MW engineering.
- **Additional circuitry** between the two parts of the original circuit may be needed to achieve this matching.


**Why is impedance matching so important?**




- ➡ **Maximum power** is delivered to a load when the TL is matched at both the load and source ends.
- ➡ With a properly matched TL, more signal power is transferred to the load, which increases the **sensitivity** of the device and improve the **SNR ratio** of the system.
- ➡ Some equipment (such as certain amplifiers) can be **damaged** when too much power is reflected back to the source.
- ➡ **Minimize** reflections.
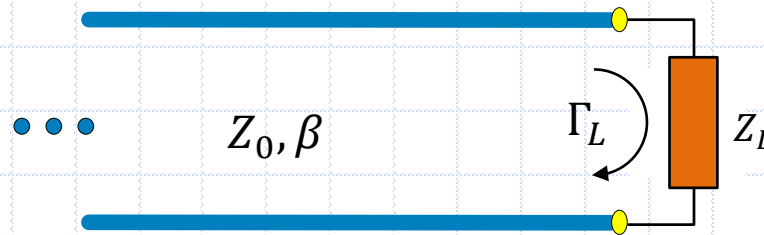
# Impedance Matching

- Consider the case of an arbitrary load that terminates a T-Line:



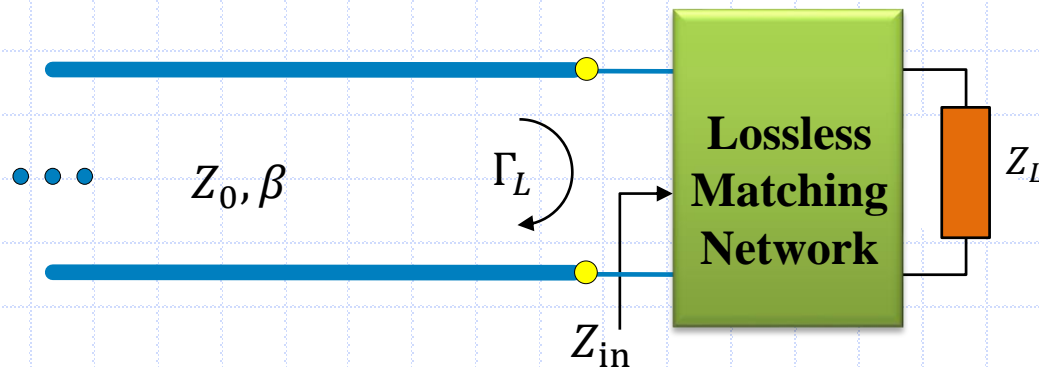- To match the load to the T-Line, we require  $\Gamma_L = 0$ .
- However, if  $Z_L \neq Z_0$ , **additional circuitry** must be placed between  $Z_L$  and  $Z_0$  to bring the VSWR = 1, or least approximately so:




✍ For  $\Gamma_L = 0$ , this implies  $Z_{in} = Z_0$ . In other words,  $R_{in} = \Re[Z_0]$  and  $X_{in} = 0$ , if the TL is lossless.
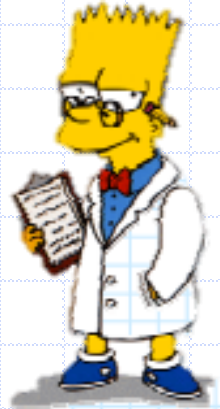
# Impedance Matching


■ We will discuss **three methods** for impedance matching in this course:

- ➡ Matching with **L-Sections** (lumped elements)
- ➡ **Stub** tuners (T-line/distributed elements)
- ➡ **Quarter wave** impedance transformers.



✍ **Factors** that influence the choice of a matching network include:

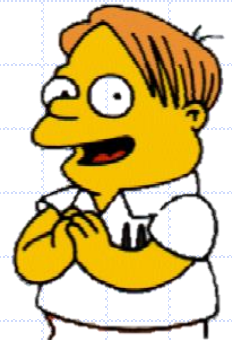- ➡ Physical complexity
- ➡ Bandwidth
- ➡ Adjustability (to match a variable load impedance)
- ➡ Implementation




# Lumped Element matching network


- Add an element in series or parallel to  $Z_L$  so that the
  - impedance at the input of the line is  $z_1 = 1 + jx$  or  $1 - jx$  (make the resistance =  $50\ \Omega$ )
  - OR admittance at the input of the line is  $y_1 = 1 + jb$  or  $1 - jb$  (make the conductance  $1/50\ \text{Si}$ ).
- Then add a lumped element in series or parallel to remove the reactive part of the impedance.
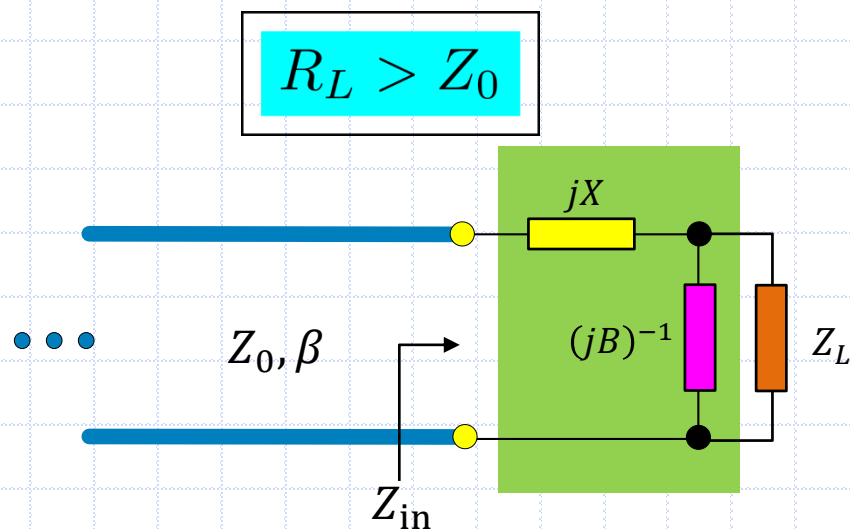
# Matching with L-Sections

- This network topology gets its **name** from the fact that the series and shunt elements of the matching network form an “**L**” shape.
- Since it uses lumped elements, it is applicable **only** if the frequency is low enough, or the circuit size is small enough
- Two possible L-Sections:


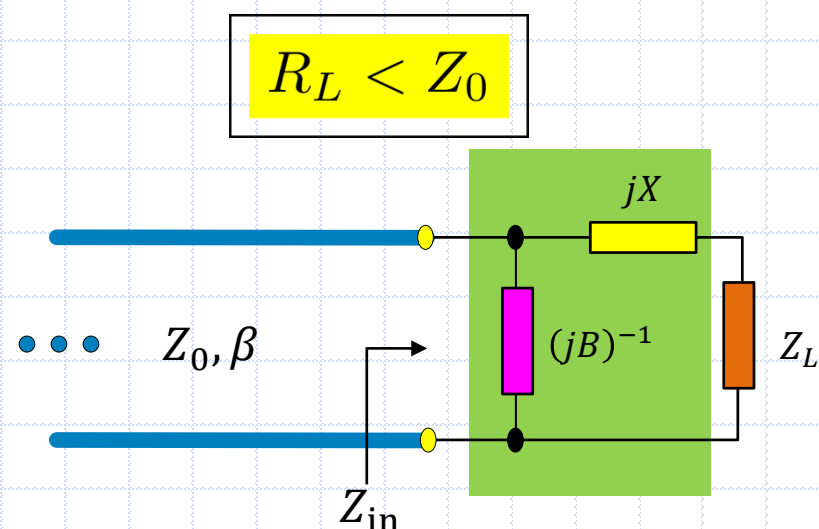
$$Z_{in} = Z_0 = jX + \underbrace{\left( jB + \frac{1}{R_L + jX_L} \right)}_{Z_L}^{-1}$$




$$Z_{in} = Z_0 = \underbrace{\left( jB + \frac{1}{Z_L + jX} \right)}_{Z_L}^{-1}$$
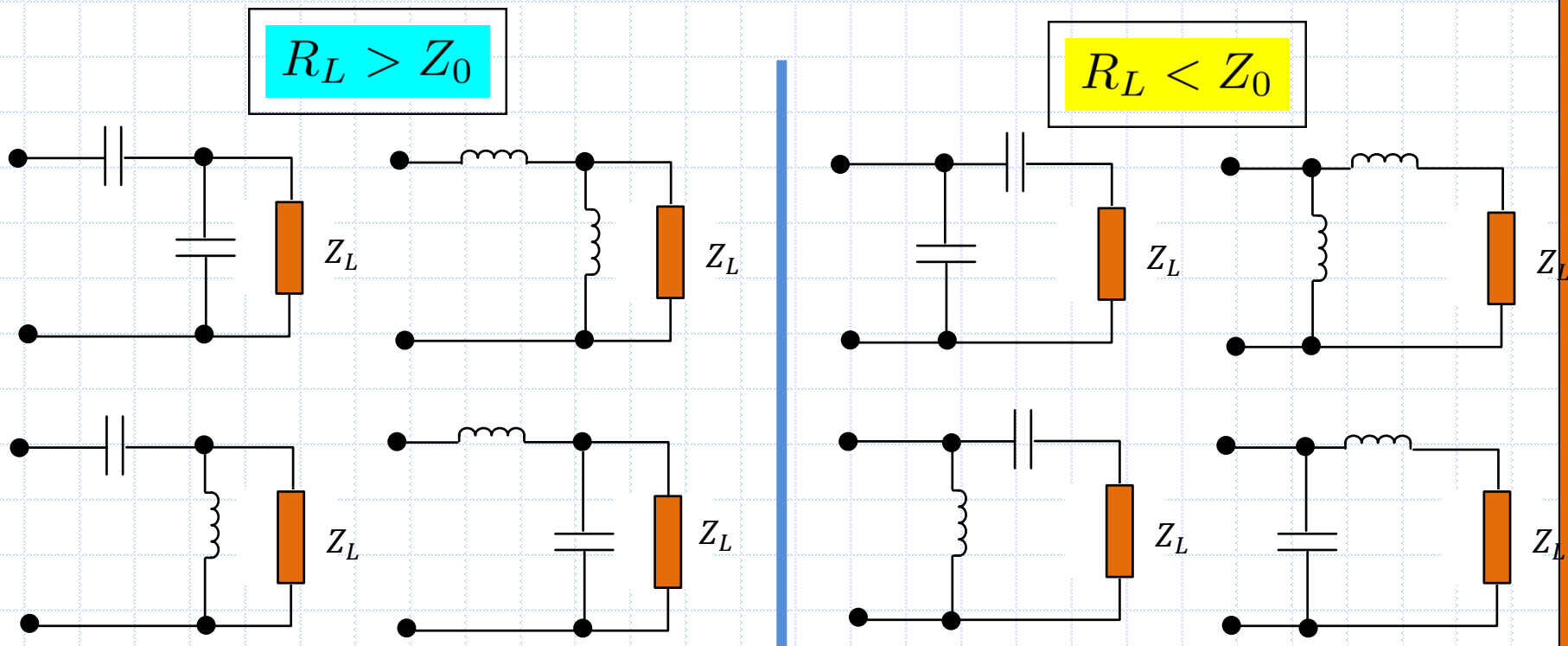
# Matching with L-Sections

There are **eight possible combinations** of inductors and capacitors in the L network:


- ➡ If  $X > 0$ ,  $X$  is an inductor; if  $X < 0$ ,  $X$  is a capacitor
- ➡ If  $B > 0$ ,  $B$  is an capacitor; if  $B < 0$ ,  $B$  is an inductor


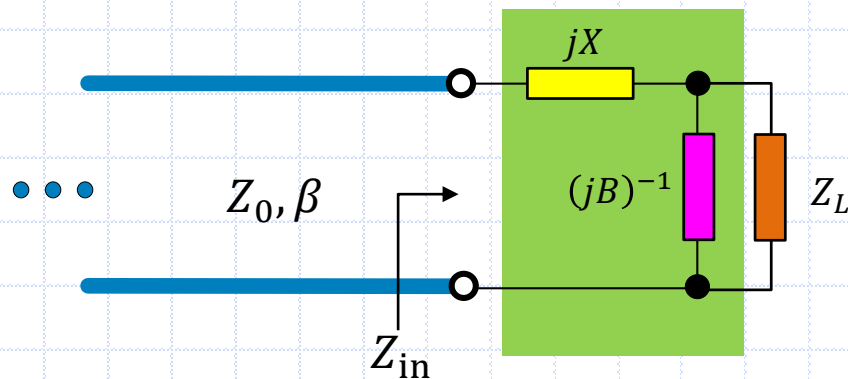
# Example 5.1

- **Design an L-section matching network to match a load with an impedance  $Z_L = 200 - j100 \Omega$  to a  $100 \Omega$  line at a frequency of 500 MHz.**

✎ Since  $R_L > Z_0$ , we'll use the following circuit topology:



$$Z_{in} = Z_0 = jX + \underbrace{\left( jB + \frac{1}{R_L + jX_L} \right)}_{Z_L}^{-1}$$

✎ **Normalization:**  $Z_L = \frac{Z_L}{Z_0} = 2 - j1 \text{ p.u.}\Omega$



# First solution

Rotated  $1 + jx$  circle  
on admittance chart  
i.e.,  $y = 1 + jb$

$1 + jx$  impedance  
circle, i.e.  $z = 1 + jx$

$$jb = +j0.3$$

$$y_1 = 0.4 + j0.5$$


$$y_L = 0.4 + j0.2$$

$$z_L = 2.0 - j1.0$$

$$z_1 = 1 - j1.2$$

$$jx = +j1.2$$

Constant VSWR  
circle

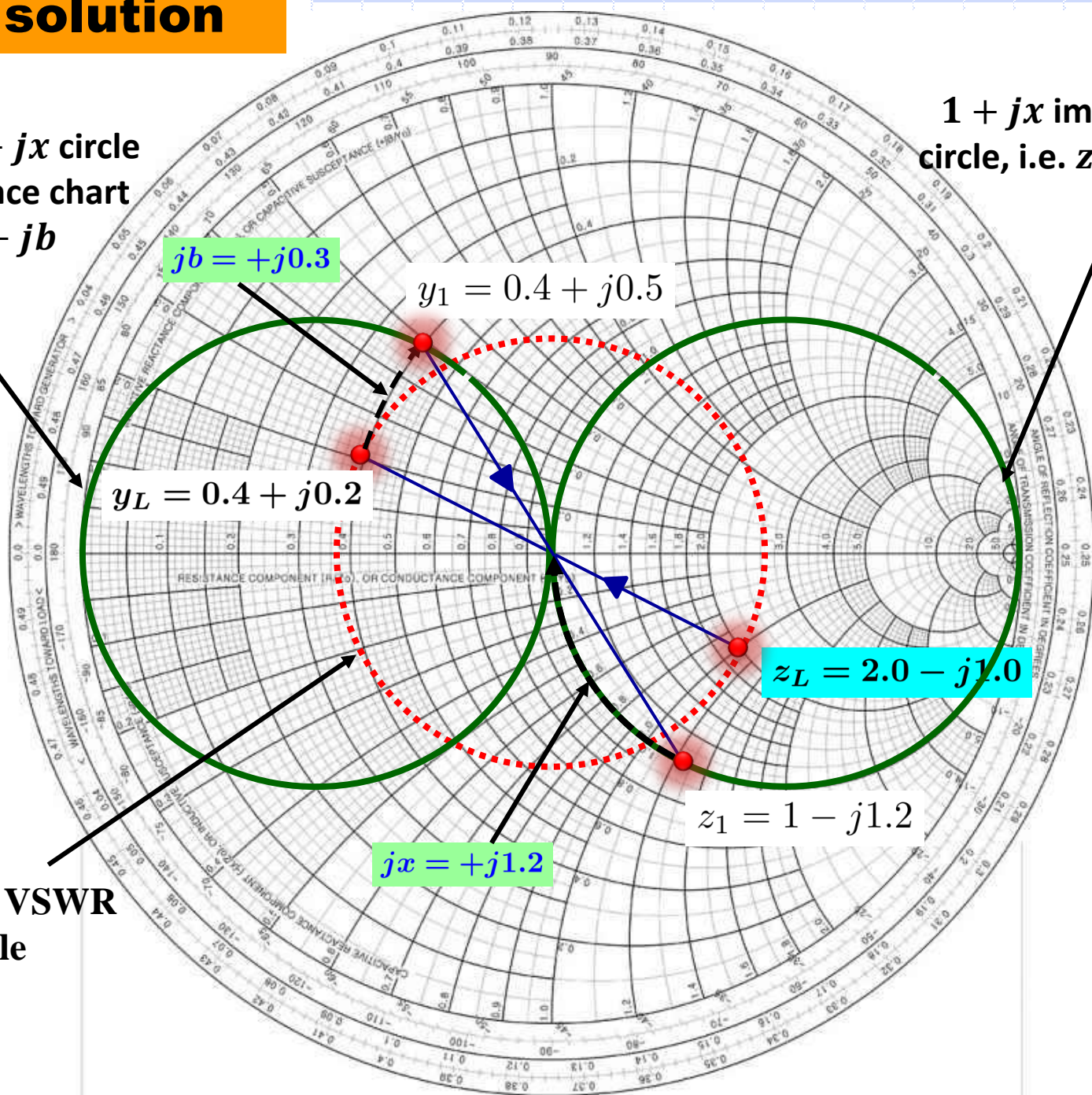

# Solution


- Un-normalizing, we find that

$$jB = jb \cdot Y_0 = j0.3 \cdot \frac{1}{100} = j0.003 \text{ S}$$

$$jX = jx \cdot Z_0 = j1.2 \cdot 100 = j120 \text{ } \Omega$$

✎ What are the L and C values of these elements?

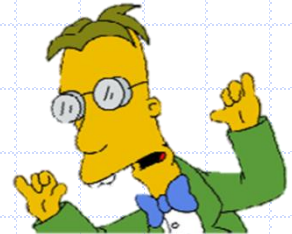- ➡ We can identify the type of element by the **sign of the reactance or susceptance**:



	Inductor	Capacitor
$X$	$Z_L = j\omega L$	$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$
$B$	$Y_L = \frac{1}{j\omega L} = \frac{-j}{\omega L}$	$Y_C = j\omega C$

# Solution

- Since  $B > 0$ , we identify this as a **capacitor**. Therefore,

$$jB = j\omega C = j0.003 \text{ S}$$


- ✎ For operation at 500 MHz, we need  $C = \frac{0.003}{2\pi f} = 0.95 \text{ pF}$

- ✎ Since  $X > 0$ , we identify this as a **inductor**. Therefore,

$$jX = j\omega L = j120 \text{ } \Omega$$

- ✎ For operation at 500 MHz, we need  $L = \frac{120}{2\pi f} = 38.8 \text{ nH}$

**The final circuit is:**

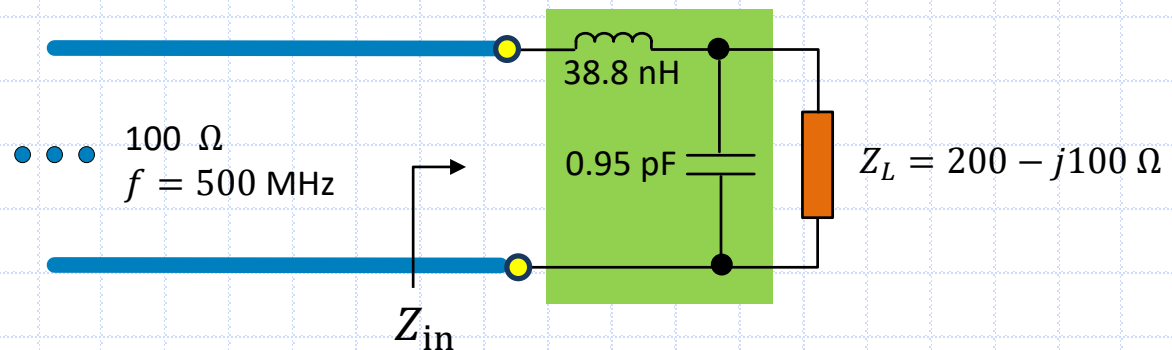


- ✎ Let's check to see if we have really achieved a match at 500 MHz:

$$\begin{aligned} Z_{in} &= j2\pi fL + \left( j2\pi fC + \frac{1}{Z_L} \right)^{-1} \\ &= j120 + 100 - j120 = 100 + j0\Omega \end{aligned}$$



# Second solution

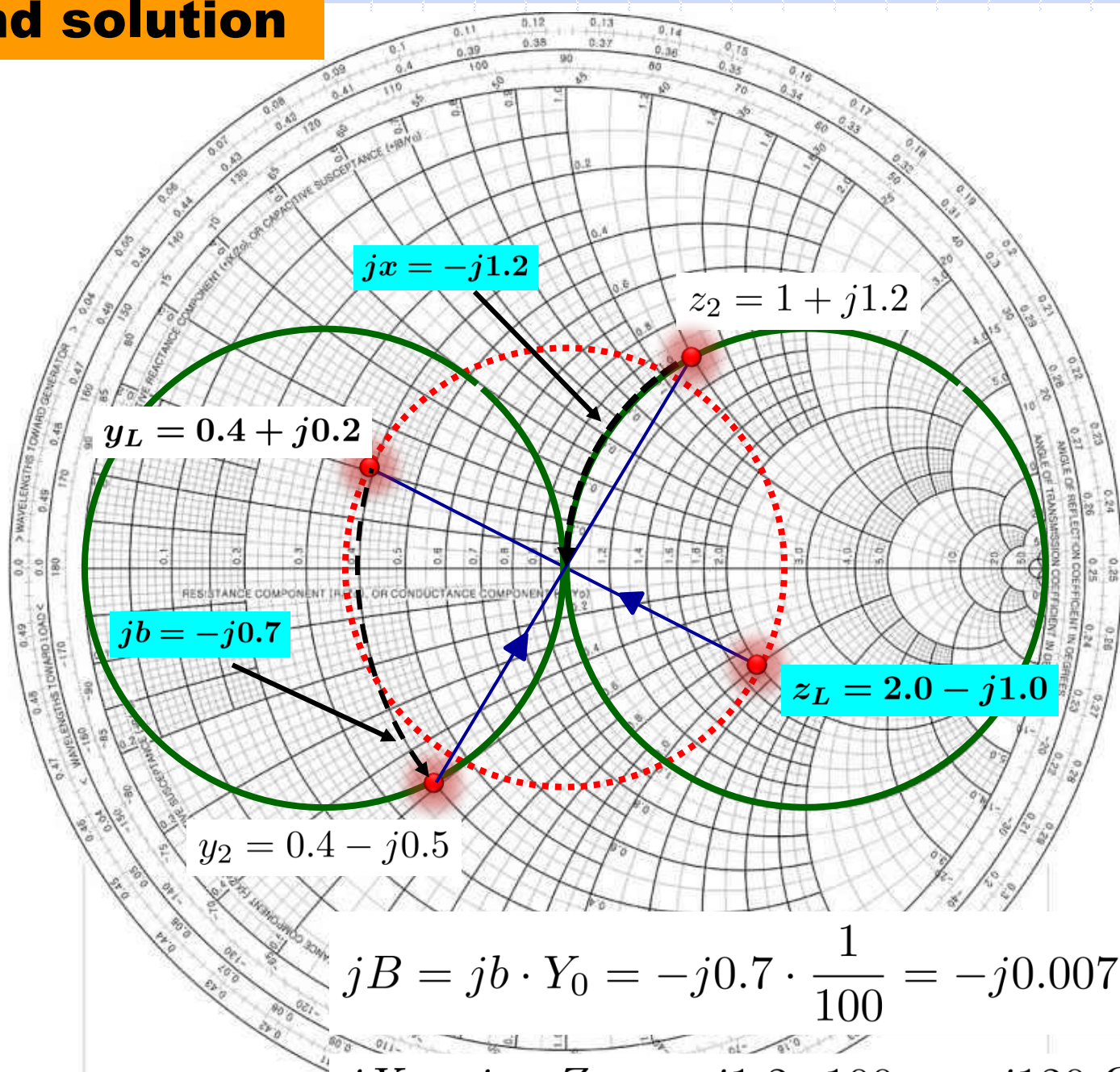

$$jB = jb \cdot Y_0 = -j0.7 \cdot \frac{1}{100} = -j0.007 \text{ S}$$

$$jX = jx \cdot Z_0 = -j1.2 \cdot 100 = -j120 \text{ } \Omega$$

# Solution

■ Since  $B < 0$ , we identify this as a **inductor**. Therefore,

$$jB = \frac{-j}{\omega L} = -j0.007 \text{ S}$$

✎ For operation at 500 MHz, we need  $L = \frac{1}{2\pi f B} = 45.47 \text{ nH}$


✎ Since  $X < 0$ , we identify this as a **capacitor**. Therefore,

$$jX = \frac{-j}{\omega C} = -j120 \text{ } \Omega$$

✎ For operation at 500 MHz, we need

$$C = \frac{1}{2\pi f X} = 2.65 \text{ pF}$$


**The final circuit is:**

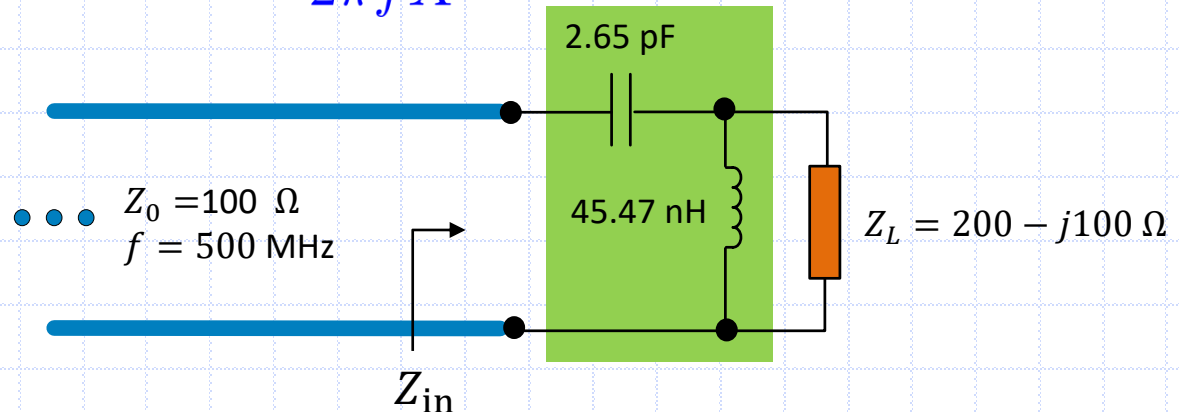


# Single-Stub Tuner (SST) Matching

- The SST uses a **shorted or open section** of T-Line attached at **some position** along another T-Line.
- It does **not** require lumped elements.
- It can be used for **extremely high** frequencies.
- It uses segments of T-lines with the **same  $Z_0$  (not necessary)** used for the feeding line.
- **Easy** to fabricate, the length can easily be made **adjustable** and little to **no power is dissipated** in the stub. (An open stub is sometimes easier to fabricate than a short.)
- It is **very convenient** for microstrip and stripline technologies.


## Stripline

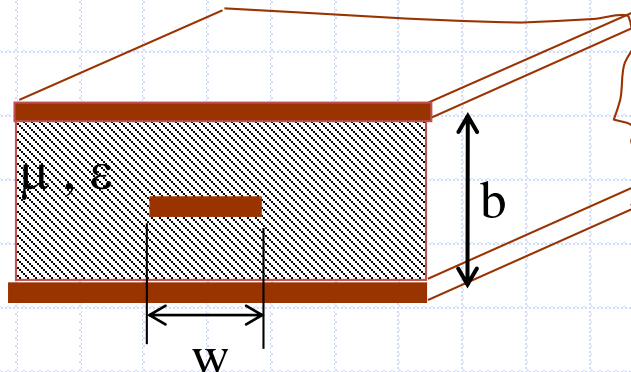

## Microstrip line

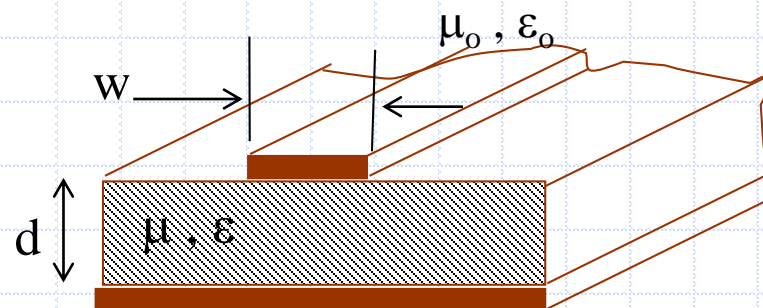

# Single-Stub Shunt Matching

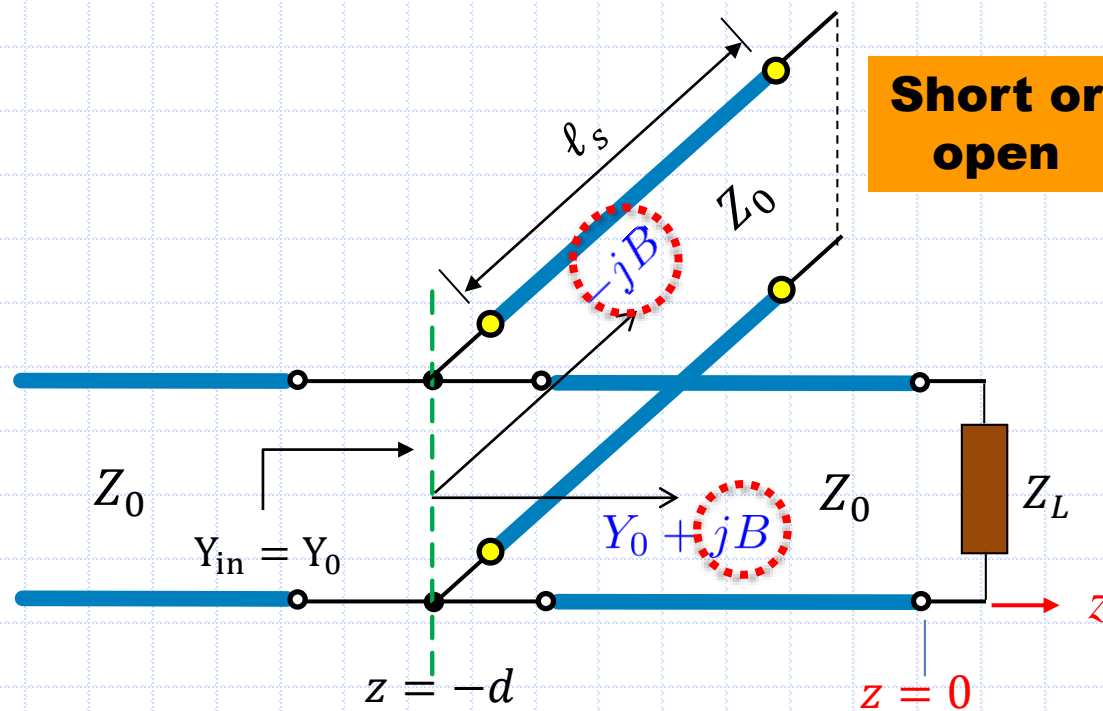

**Short or open**

We only need to find  $d$  and  $\ell_s$




First T-Line converts  $Y_L = 1/Z_L$  to an admittance  $Y_0 + jB$

Second T-Line converts a short or an open to an admittance  $-jB$



# Single-Stub Series Matching

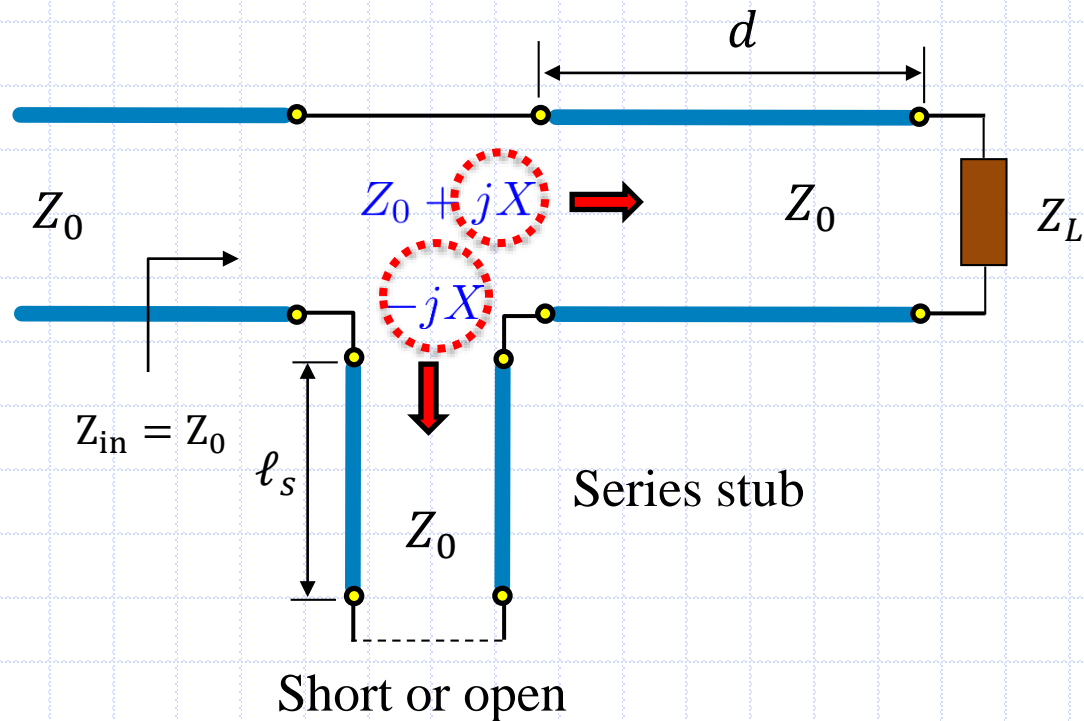

- # **First** T-Line converts  $Z_L$  to an impedance  $Z_0 + jX$
- # **Second** T-Line converts a short or an open to an impedance  $-jX$
- # We only need to find  $d$  and  $\ell_s$


# SST Using the Smith Chart

■ In terms of quantities **normalized** to  $Z_0$  or  $Y_0$ , the geometry is

✎ Recall that the operation of the SST requires that

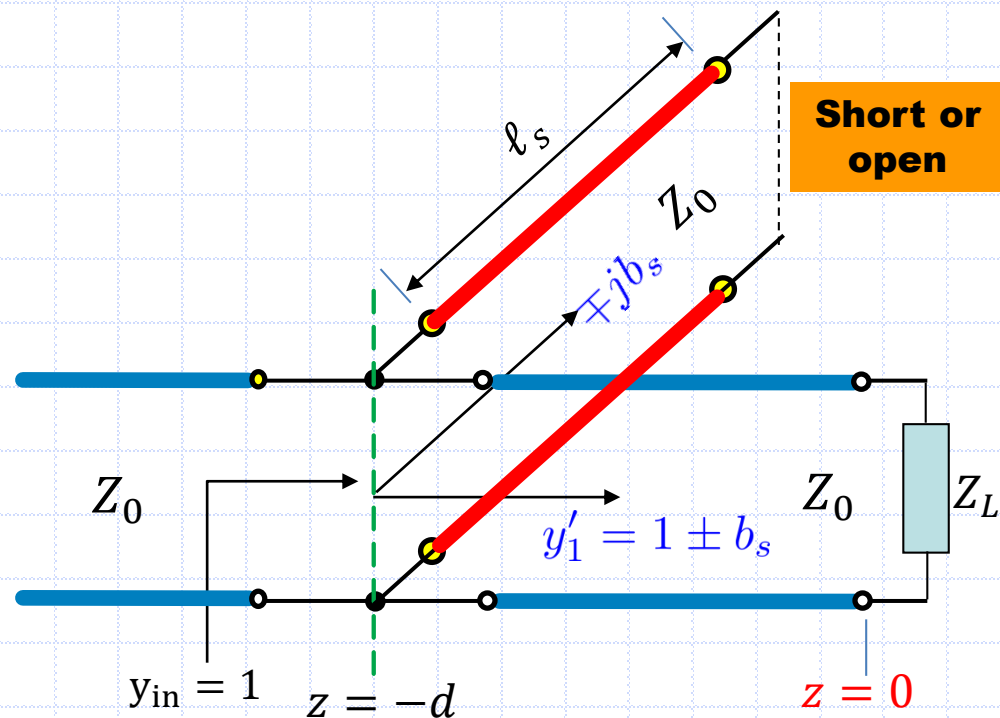1.  $d$  is chosen such that  $y'_1$  has a **real part = 1**, i.e.,  $y'_1 = 1 \pm jb_s$ .
2. The imaginary part of  $y'_1$  is **removed** by the stub susceptance after choosing the proper length  $\ell_s$ .


✎ This produces  $y_{in} = 1$ , which is the **matched state**.



✎ **Example 5.2: Using the Smith chart, design a shorted shunt, single-stub tuner to match the load  $Z_L = 60 - j80 \Omega$  to a T-Line with characteristic impedance  $Z_0 = 50 \Omega$ .**


✎ The normalized load impedance is:  $z_L = 1.2 - j1.6$  p.u. $\Omega$

# First solution

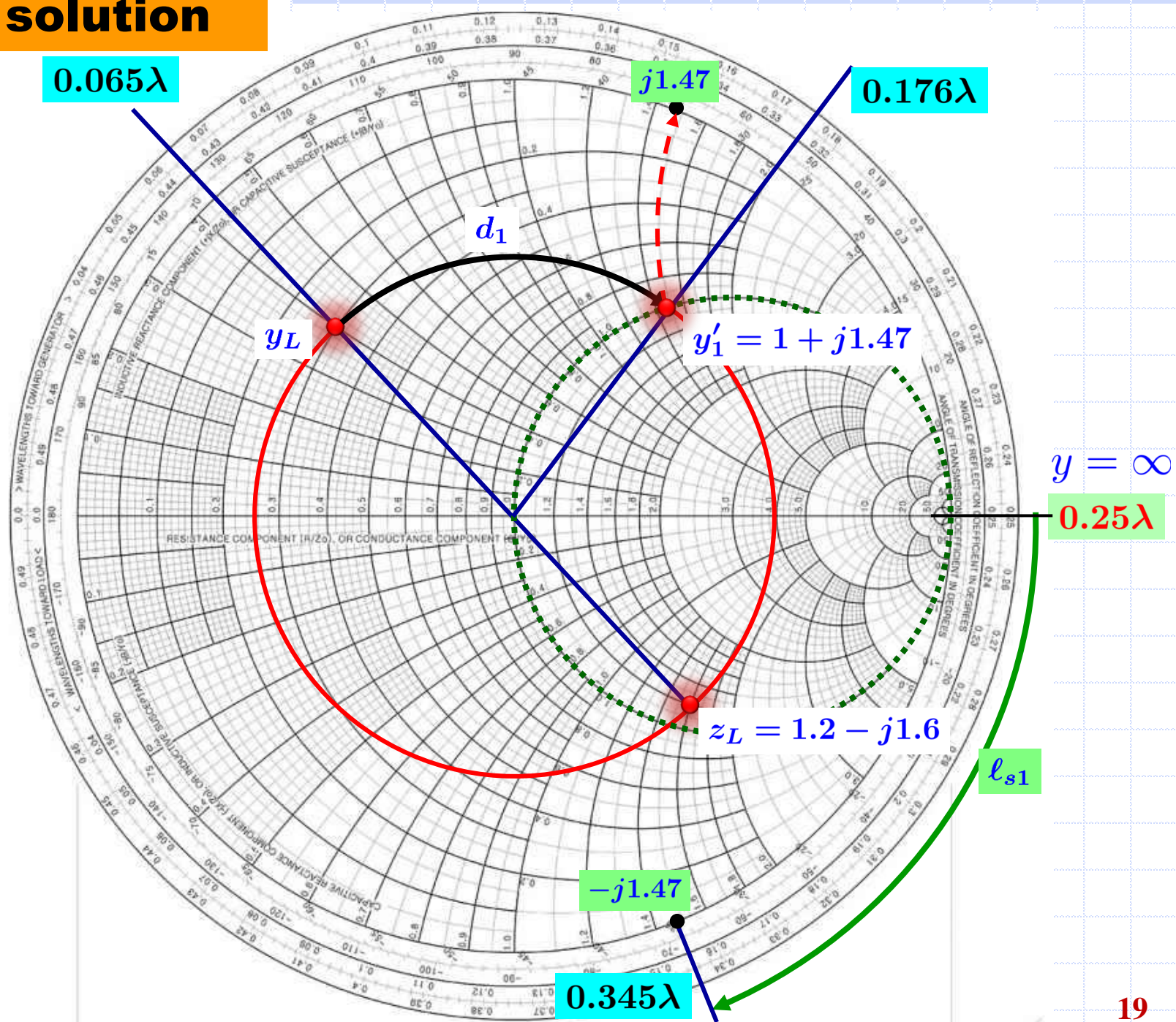



## Second solution

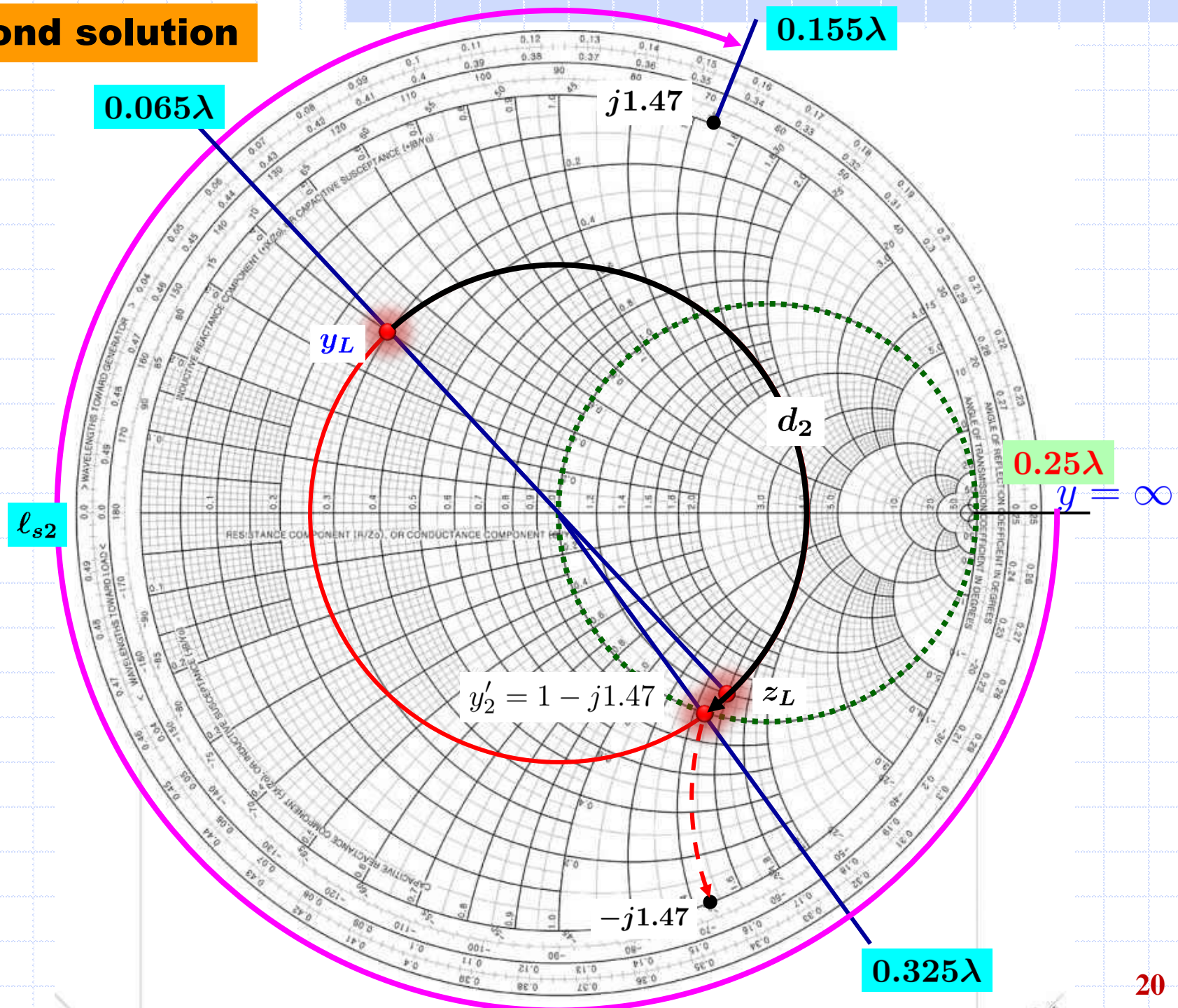

# Solution: Smith

■ There will be **two solutions**. Both of these give  $y' = 1 \pm jb_s$ .

■ For this example, we find from the Smith chart that

(I)  $y'_1 = 1 + j1.47$

(II)  $y'_2 = 1 - j1.47$

■ From these rotations we can compute  $d$  as

(I)  $d_1 = 0.176\lambda - 0.065\lambda = 0.110\lambda$

(II)  $d_2 = 0.325\lambda - 0.065\lambda = 0.260\lambda$

■ Next, find the stub lengths  $\ell_s$ :


(I) want  $b_{s1} = -1.47$

(II) want  $b_{s2} = 1.47$

When either of these two susceptances is added to  $y'_1$ , then  $y_{in} = 1$ .
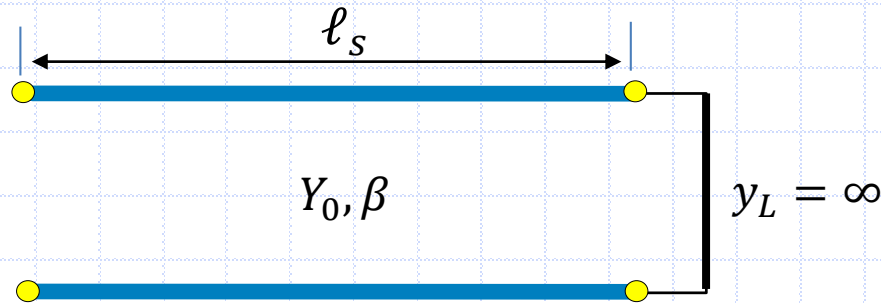
# Solution: Smith

The stub lengths can be determined directly from the Smith chart.



On the Smith admittance chart,  $y_L = \infty$  is located at  $\Re\{\Gamma\} = 1$ ,  $\Im\{\Gamma\} = 0$ . From there, rotate “wavelengths towards generator” to:

$$(I) b_s = -1.47 \Rightarrow \ell_{s1} = 0.345\lambda - 0.25\lambda = 0.095\lambda$$



$$(II) b_s = +1.47 \Rightarrow \ell_{s2} = 0.25\lambda + 0.155\lambda = 0.405\lambda$$

The final two solutions are:

$$(I) d_1 = 0.110\lambda \text{ and } \ell_{s1} = 0.095\lambda$$

$$(II) d_2 = 0.260\lambda \text{ and } \ell_{s2} = 0.405\lambda$$

# Solution: Smith

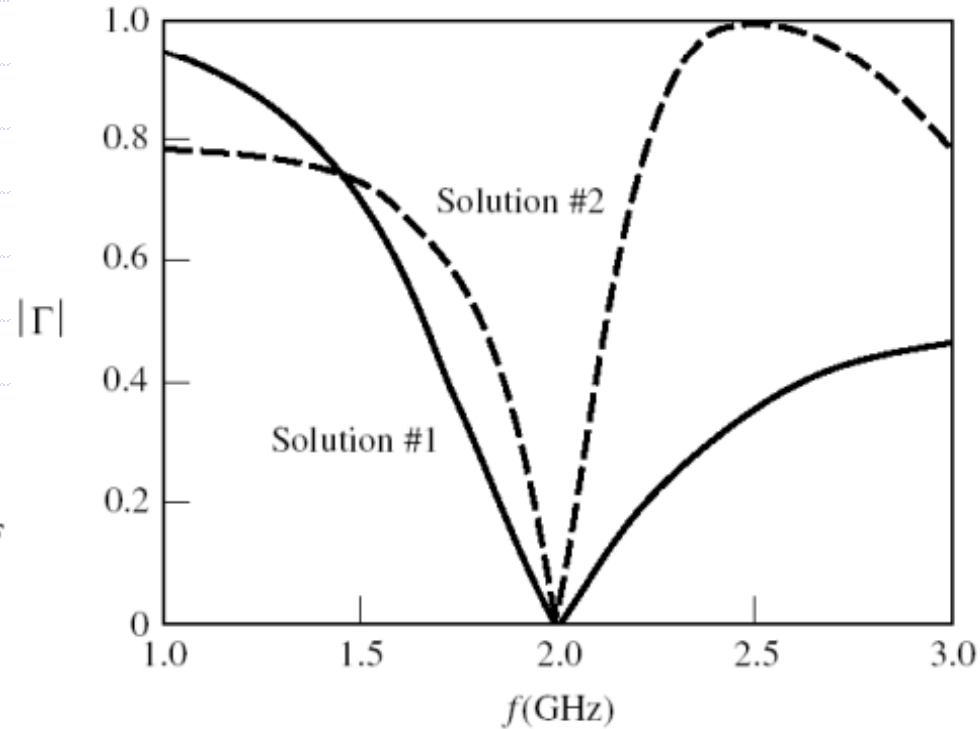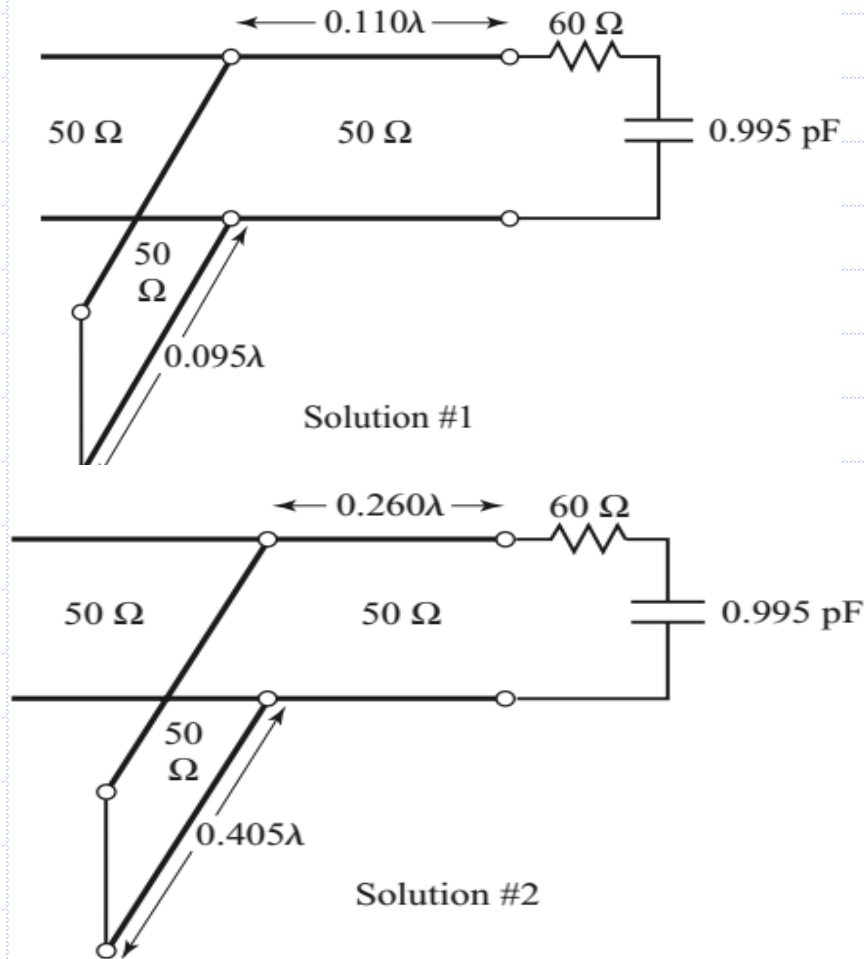

- Solution 1** has a significantly better bandwidth than solution 2.
- Shorter stub produces wider bandwidth.

# Thank you



# Have a nice day.

